




## AP Physics B 2000 Student Samples

**The materials included in these files are intended for non-commercial use by AP teachers for course and exam preparation; permission for any other use must be sought from the Advanced Placement Program. Teachers may reproduce them, in whole or in part, in limited quantities, for face-to-face teaching purposes but may not mass distribute the materials, electronically or otherwise. These materials and any copies made of them may not be resold, and the copyright notices must be retained as they appear here. This permission does not apply to any third-party copyrights contained herein.**

These materials were produced by Educational Testing Service (ETS), which develops and administers the examinations of the Advanced Placement Program for the College Board. The College Board and Educational Testing Service (ETS) are dedicated to the principle of equal opportunity, and their programs, services, and employment policies are guided by that principle.

The College Board is a national nonprofit membership association dedicated to preparing, inspiring, and connecting students to college and opportunity. Founded in 1900, the association is composed of more than 3,900 schools, colleges, universities, and other educational organizations. Each year, the College Board serves over three million students and their parents, 22,000 high schools, and 3,500 colleges, through major programs and services in college admission, guidance, assessment, financial aid, enrollment, and teaching and learning. Among its best-known programs are the SAT<sup>®</sup>, the PSAT/NMSQT<sup>™</sup>, the Advanced Placement Program<sup>®</sup> (AP<sup>®</sup>), and Pacesetter<sup>®</sup>. The College Board is committed to the principles of equity and excellence, and that commitment is embodied in all of its programs, services, activities, and concerns.

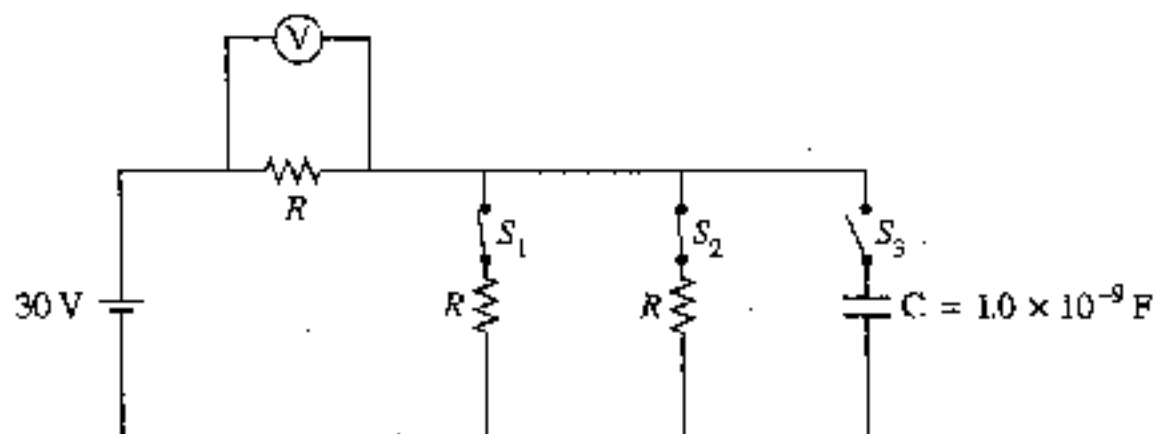Copyright © 2001 by College Entrance Examination Board. All rights reserved. College Board, Advanced Placement Program, AP, and the acorn logo are registered trademarks of the College Entrance Examination Board.



3. (15 points)

Three identical resistors, each with resistance  $R$ , and a capacitor of  $1.0 \times 10^{-9} \text{ F}$  are connected to a  $30 \text{ V}$  battery with negligible internal resistance, as shown in the circuit diagram above. Switches  $S_1$  and  $S_2$  are initially closed, and switch  $S_3$  is initially open. A voltmeter is connected as shown.

(a) Determine the reading on the voltmeter.

$$\begin{aligned}
 & 30\text{V} \text{ --- } R \text{ --- } \left( \frac{1}{2}R \right) \Rightarrow 30\text{V} \text{ --- } \left[ \begin{array}{c} R \\ R \end{array} \right] \text{ --- } \frac{1}{2}R \\
 & V = IR \quad (30\text{V}) = I \left( \frac{1}{2}R \right) \\
 & I = \frac{20\text{V}}{R} \quad \begin{array}{c} A \text{ --- } R \text{ --- } B \end{array} \\
 & I = \frac{20\text{V}}{R} \quad V = IR \quad V = \left( \frac{20\text{V}}{R} \right) R = \boxed{20\text{V}}
 \end{aligned}$$


(b) Switches  $S_1$  and  $S_2$  are now opened, and then switch  $S_3$  is closed. Determine the charge  $Q$  on the capacitor after  $S_3$  has been closed for a very long time.

$$C = \frac{Q}{V} \quad Q = VC \quad V = 30\text{V} \quad C = 1 \times 10^{-9}$$

$$\underline{\underline{3 \times 10^{-8} \text{ C}}}$$

GO ON TO THE NEXT PAGE.

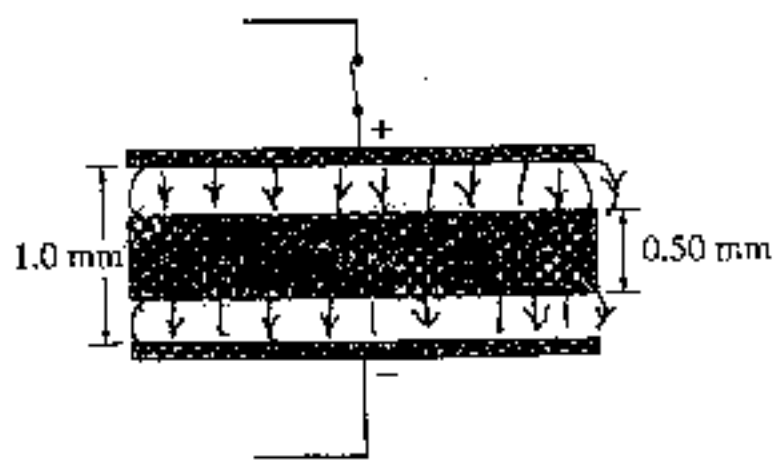After the capacitor is fully charged, switches  $S_1$  and  $S_2$  remain open, switch  $S_3$  remains closed, the plates are held fixed, and a conducting copper block is inserted midway between the plates, as shown below. The plates of the capacitor are separated by a distance of 1.0 mm, and the copper block has a thickness of 0.5 mm.



- (c) i. What is the potential difference between the plates?

30 V


- ii. What is the electric field inside the copper block?

0

- iii. On the diagram above, draw arrows to clearly indicate the direction of the electric field between the plates.

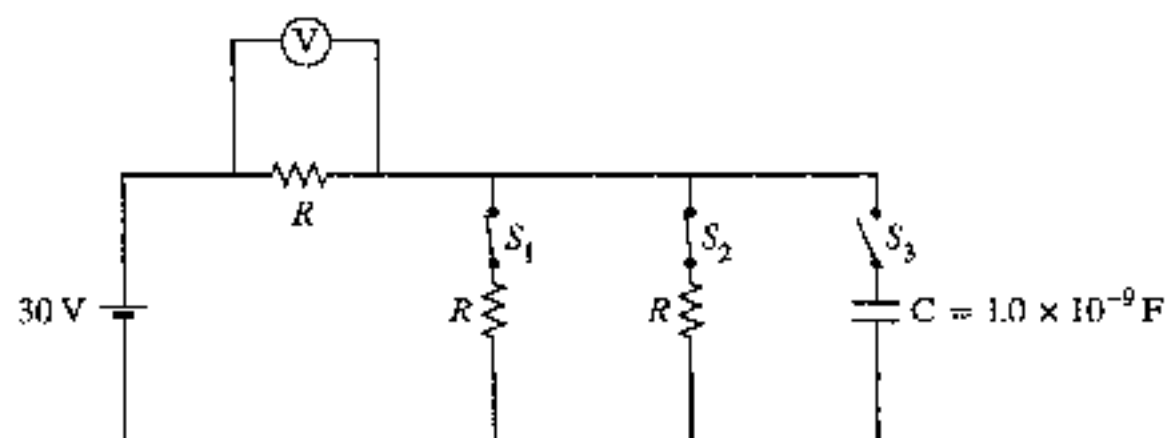- iv. Determine the magnitude of the electric field in each of the spaces between the plates and the copper block.

$$E = \frac{V}{d} = \frac{30V}{0.5mm} = \frac{30V}{.0005m} = 60,000 \frac{V}{m}$$



3. (15 points)

Three identical resistors, each with resistance  $R$ , and a capacitor of  $1.0 \times 10^{-9} \text{ F}$  are connected to a 30 V battery with negligible internal resistance, as shown in the circuit diagram above. Switches  $S_1$  and  $S_2$  are initially closed, and switch  $S_3$  is initially open. A voltmeter is connected as shown.

(a) Determine the reading on the voltmeter.

$$\begin{aligned} \frac{1}{R_T} &= \frac{1}{R} + \frac{1}{R} = \frac{2}{R} = \frac{1}{R_T} \\ R_T &= \frac{R}{2} + R \\ &= \frac{3R}{2} \\ V &= IR \\ 30 &= I \frac{3R}{2} \\ I &= \frac{20}{R} \end{aligned}$$


$$\begin{aligned} V &= IR \\ &= \frac{20}{R} R \\ &= 20 \text{ V} \end{aligned}$$

(b) Switches  $S_1$  and  $S_2$  are now opened, and then switch  $S_3$  is closed. Determine the charge  $Q$  on the capacitor after  $S_3$  has been closed for a very long time.

$$\begin{aligned} Q &= CV \\ &= 1.0 \times 10^{-9} \cdot 30 \\ &= 3.0 \times 10^{-8} \text{ C} \end{aligned}$$

GO ON TO THE NEXT PAGE.

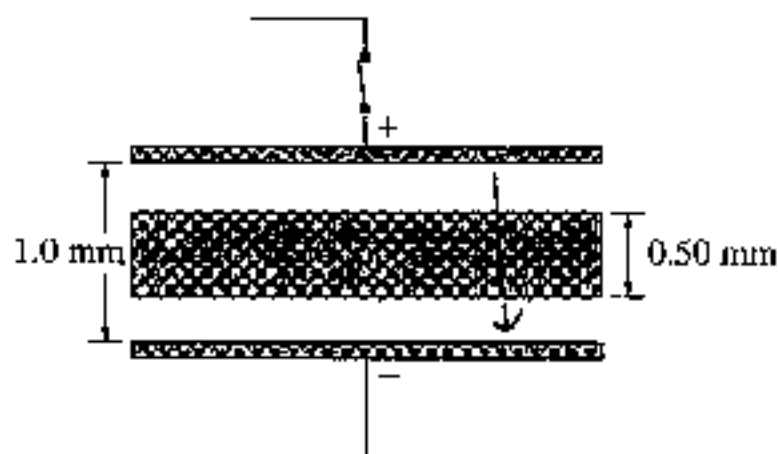After the capacitor is fully charged, switches  $S_1$  and  $S_2$  remain open, switch  $S_3$  remains closed, the plates are held fixed, and a conducting copper block is inserted midway between the plates, as shown below. The plates of the capacitor are separated by a distance of 1.0 mm, and the copper block has a thickness of 0.5 mm.



- (c) i. What is the potential difference between the plates?

$$V = 30 \text{ V} //$$

- ii. What is the electric field inside the copper block?


$$E = \frac{V}{d} = \frac{30}{1.0 \times 10^{-3}} = 3.0 \times 10^4 \frac{\text{N}}{\text{C}} //$$

- iii. On the diagram above, draw arrows to clearly indicate the direction of the electric field between the plates.

- iv. Determine the magnitude of the electric field in each of the spaces between the plates and the copper block.

$$E = \frac{V}{d} = \frac{30}{0.25} = 120 \text{ N/C} //$$


N1

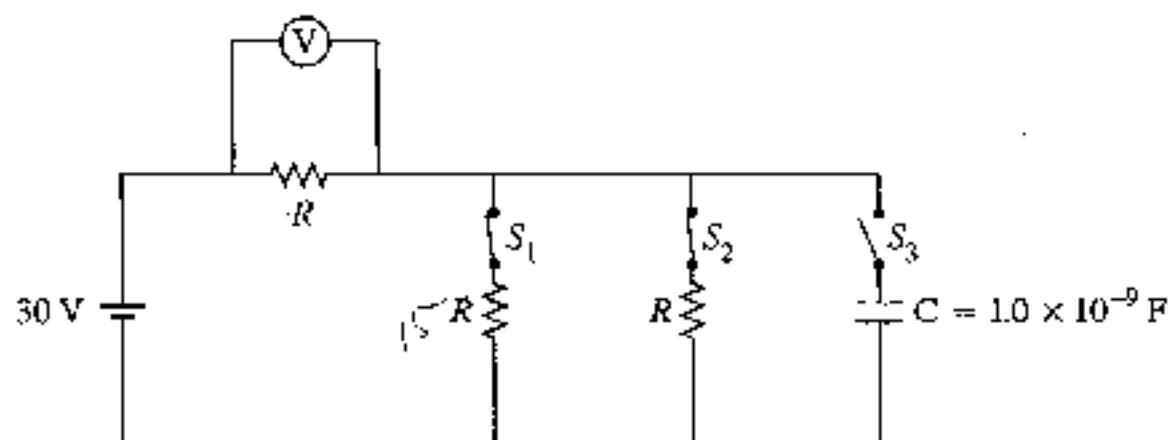

3. (15 points)

Three identical resistors, each with resistance  $R$ , and a capacitor of  $1.0 \times 10^{-9} \text{ F}$  are connected to a  $30 \text{ V}$  battery with negligible internal resistance, as shown in the circuit diagram above. Switches  $S_1$  and  $S_2$  are initially closed, and switch  $S_3$  is initially open. A voltmeter is connected as shown.

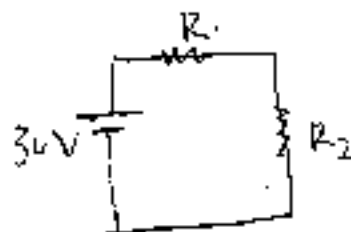(a) Determine the reading on the voltmeter.



Since  $R_1 = R_2$   
and in series, voltage is added up from  
each resistor

Thus, the reading on the voltmeter  
will be  $\frac{30}{2} = 15 \text{ V}$

(b) Switches  $S_1$  and  $S_2$  are now opened, and then switch  $S_3$  is closed. Determine the charge  $Q$  on the capacitor after  $S_3$  has been closed for a very long time.


$$C = \frac{Q}{V}$$

$$1.0 \times 10^{-9} = \frac{Q}{30}$$

$$Q = 3.0 \times 10^{-8} \text{ C}$$

GO ON TO THE NEXT PAGE.

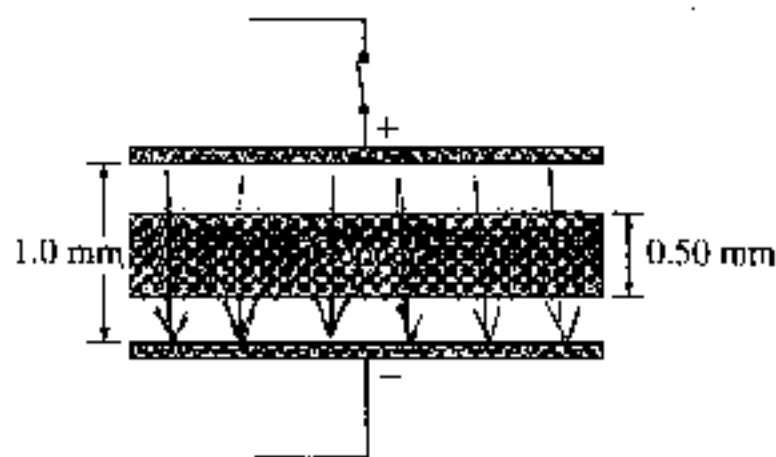After the capacitor is fully charged, switches  $S_1$  and  $S_2$  remain open, switch  $S_3$  remains closed, the plates are held fixed, and a conducting copper block is inserted midway between the plates, as shown below. The plates of the capacitor are separated by a distance of 1.0 mm, and the copper block has a thickness of 0.5 mm.



- (c) i. What is the potential difference between the plates?

$$\text{potential difference} = \text{voltage} = 30 \text{ V}$$

- ii. What is the electric field inside the copper block?

ZERO

- iii. On the diagram above, draw arrows to clearly indicate the direction of the electric field between the plates.

- iv. Determine the magnitude of the electric field in each of the spaces between the plates and the copper block.

$$E = \frac{V}{d}$$

$$E = \frac{30}{0.5} = 60 \frac{\text{V}}{\text{m}}$$